 


BLOCK DIAGRAM



FUNCTION TABLE

rst	pr	clk	dir	Q_{n+1} (Next State)	Operation
1	0	x	x	00000	Reset
0	1	x	x	11111	Set
0	0	↓	1	$Q_n + 1$	With Counter Set to $Q = 00000$ $(0)_{10} \rightarrow (24)_{10}$
0	0	↓	0	$Q_n - 1$	With Counter Preset to $Q = 11111$ $(31)_{10} \rightarrow (7)_{10}$

MAIN VHDL MODEL (MVM) / ARCHITECTURE BODY

architecture mod25_arch of mod25 is

signal Qtemp : STD_LOGIC_VECTOR (4 downto 0) := "00000";

begin

 process(rst,pr,clk,dir)

 begin

 if rst ='1' then

 Qtemp <= (OTHERS =>'0');

 elsif pr='1' then

 Qtemp <= (OTHERS =>'1');

 elsif falling_edge(clk) then

 if dir = '1' then

 if Qtemp < 24 then

 Qtemp <= Qtemp + 1;

 else

 Qtemp <= "00000";

 end if;

 else

 if Qtemp > 7 then

 Qtemp <= Qtemp - 1;

 else

 Qtemp <= "11111";

 end if;

 end if;

 end if;

 end process;

 Q<=Qtemp;

end mod25_arch;